
 


# Transistors

- The transistor is a main building block of all modern electronic systems.
- They are 3 terminal device and are of 2 types:
  - 1) **Bipolar Junction Transistor (BJT)**
  - 2) **Field Effect Transistor (FET)**

- BJT – output current, voltage and/or power is **controlled by the input current**. Conduction is due to **both e- and h+** so are called bipolar.
- FET- output characteristics are **controlled by input voltage**. Conduction is due to **either e- or h+** so are called unipolar.
- In communication systems transistors are widely used as the primary component in the Amplifier (circuit that is used to increase the strength ie: amplify, an ac signal).
- We will first consider **BJT** and look at **FET** later


# Transistors

 


# BJT

- The BJT transistor consists of 2 PN junctions and is formed from a single bar of for example Si (Group 14 SPT), that has been doped in the proper way.
- There are two ways to arrange the 2 PN junctions:



NPN Type

 


PNP Type

 

 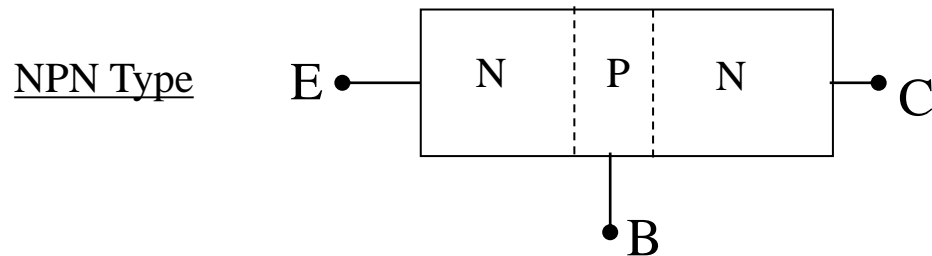- The BJT has essentially 3 regions known as Emitter (E), Base (B) and Collector (C).
- All three regions are provided with terminals.
- The junction between the Emitter and Base is known as the Emitter-Base (E-B) junction
- The junction between the Collector and Base is known as the Collector-Base (C-B) junction




- **Emitter:** supplies charge carriers ( $e^-$  and  $h^+$ ) to the other two regions – this is a **heavily doped** region
- **Base:** Middle region that forms the 2 PN junctions. The base of the transistor is thin as compared to the E and is a **lightly doped** region
- **Collector:** collects the charge carriers ( $e^-$  and  $h^+$ ). Always larger than the E and B. Its **doping is intermediate** between the E and B.

 

- **Circuit Symbols:** (Arrow points from P to N and indicates direction of conventional current flow).
- PNP transistor is a complement of NPN.
- NPN- majority carriers are free e-.
- PNP- majority carriers are h+.
- We will discuss in terms of NPN. For PNP reverse direction of current and polarity of supplies
 
# Unbiased Transistor



- Transistor with E, B and C terminals left open is called an unbiased transistor or open-circuited transistor.
- Diffusion across the PN junctions produce 2 depletion layers.
- **E-B depletion layer:** penetrates slightly into the Emitter (heavily doped) but deeply into the Base (lightly doped).
- **C-B depletion layer:** penetrates more into the Base (lightly doped) and less into the Collector (intermediate doping between E and B).
- E-B depletion layer width is smaller than that of the C-B depletion layer.





- An unbiased transistor is never used in practice.
- In practice all terminals are connected to DC voltage sources (or batteries).
- For proper transistor action it is necessary to bias both PN junctions.
- We first look at biasing the NPN transistor in Common Base configuration.

# Common Base Configuration

  

i) E-B Junction – Forward Biased by DC source  $V_{EE}$ .

ii) –ve terminal of  $V_{EE}$  connected to N or E, +ve terminal of  $V_{EE}$  connected to P or B

iii) Substantial flow of diffusion current across junction due to flow of majority carriers (e-) from N type E


C-B junction is reverse biased by DC source  $V_{CC}$ .

+ve terminal of  $V_{CC}$  to N or C,  
–ve terminal of  $V_{CC}$  to P or B

Depletion layer is widened and only current flow from B to C is due to the minority e- crossing the junction

 
**Rule for Biasing: E-B junction FB; C-B junction RB**

- Rule for Biasing: E-B junction FB; C-B junction RB



$$I_E = I_C + I_B$$
 
## Common-Base Transistor Gain and $I_{CBO}$ :



- If Emitter is open. No carriers injected to Base from E.
- The only current that flows is due to thermally generated carriers.
- This current is called reverse saturation current and designated as  $I_{CBO}$  the Collector to Base current with Emitter open.
- NB:  $I_{CBO}$  can be considered same as the reverse diode current.
- Total collector current  $I_c$  consists of
  - 1) current produced by normal transistor action called injected current  $I_c(INJ)$ , and
  - 2) Reverse saturation current  $I_{CBO}$ .
- Therefore total collector current  $I_c = I_c(INJ) + I_{CBO}$

- Important parameter

$$\alpha = I_c(\text{INJ}) / I_E$$

measures portion of Emitter current that pass through the Base to become Collector current.

- $\alpha$  is always  $< 1$
- Greater the value of  $\alpha$  (the closer it is to 1) the better the transistor.
- For typical transistors  $\alpha = 0.95$  to  $0.995$ .

$$I_c(\text{INJ}) = \alpha I_E \text{ and therefore } I_c = \alpha I_E + I_{\text{CBO}}$$


- Value of  $I_{\text{CBO}}$  is usually very small compared to  $I_E$ , so
- $I_c = \alpha I_E$  or
- $\alpha = I_c / I_E$  and is called the **Common-Base DC current gain**

# Transistor Characteristics


- 1) **Input Characteristics**: gives relationship between the input current and input voltage for a given output voltage,
- 2) **Output Characteristics**: gives relationship between the output current and voltage for a given input current.

# Common Base Characteristics

Input/output voltages and currents


 


Input Characteristics

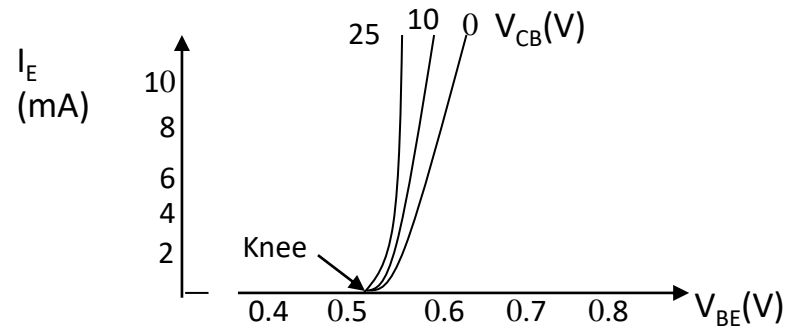

- (1) There is a threshold voltage (knee, offset, cut-in) below which Emitter current is very small [ this voltage is 0.7V(Si), 0.3V(Ge)],
- (2) Beyond the knee for fixed  $V_{CB}$ ,  $I_E$  increase rapidly with  $V_{BE}$   
Means the input resistance is small
- (3) As  $V_{CB}$  increases the curves shift upwards,
  - Can determine the value of ac resistance  $R_i = \Delta V_{BE} / \Delta I_E$
  - The ac input resistance depends on the location of the operating point selected along the curve.


# Common-Base Output Characteristics:

 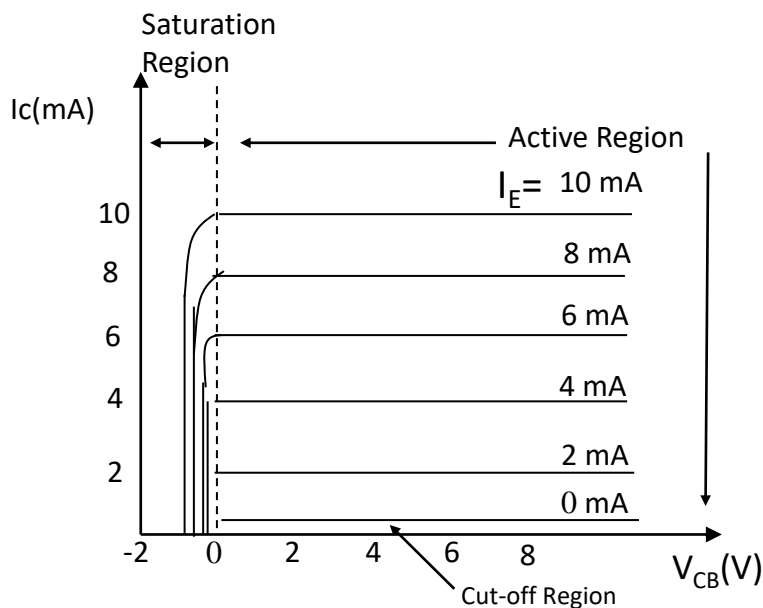

- (1) Curves may be divided into three regions: saturation, active and cut-off regions.
  - (a) **Saturation** :  $V_{CB}$  is negative for NPN transistor. Means C-B junction is also FB.
  - (b) **Active** : Collector current is constant and nearly equal to Emitter Current ( $\alpha \approx 1$ ),
  - (c) **Cut-off**: Along the horizontal axis. Correspond to  $I_E = 0$ . Both junctions RB.
- (2) Collector current flows even when  $V_{CB}$  is zero. This is due to  $e^-$  being injected into the base under the FB E-B junction. These  $e^-$  reach Collector due to internal junction barrier potential.
- (3) A small current flows for  $I_E = 0$  this is the  $I_{CBO}$



# Common Emitter Configuration:

 

- Previous eqns

$$I_C = \alpha I_E + I_{CBO}$$


$$I_C / \alpha - I_{CBO} / \alpha = I_E = I_C + I_B$$

$$I_C (1 / \alpha - 1) = I_B + I_{CBO} / \alpha$$

$$I_C = \alpha I_B / (1 - \alpha) + I_{CBO} / (1 - \alpha) = \beta I_B + I_{CBO} / (1 - \alpha)$$

$\beta = \alpha / (1 - \alpha)$  is the Common-Emitter DC current gain.

 
$\beta$  is always  $> 1$ , and ranges from 20 to several hundred.





- Fig ( c ): Base-Emitter circuit left open while RB ( $V_{CC}$ ) remains connected.
- The only current that can flow is the reverse current across Collector-Base junction.
- Current flows from C through B to E.
- This is designated  $I_{CEO}$ , the Collector to Emitter current when Base is open.
- NB:  $I_{CEO}$  is in the same direction as  $I_C$ .
- Since  $I_B = 0$ ,  $I_{CEO} = [1/(1-\alpha)] I_{CBO}$ .
- As  $\alpha$  is close to 1,  $(1-\alpha)$  is close to zero and  $1/(1-\alpha)$  can be quite large.
- So the Common Emitter leakage current  $\gg$  Common Base leakage current.
- $I_C = \beta I_B + I_{CBO}/(1-\alpha) = \beta I_B + I_{CEO}$ .
- Although  $I_{CEO} \gg I_{CBO}$ , it is still very small compared to  $\beta I_B$ .
- Therefore,  $I_C = \beta I_B$  and  $\beta = I_C/I_B$

# Common-Emitter Characteristics

Input Characteristics

 

Output Characteristics

 
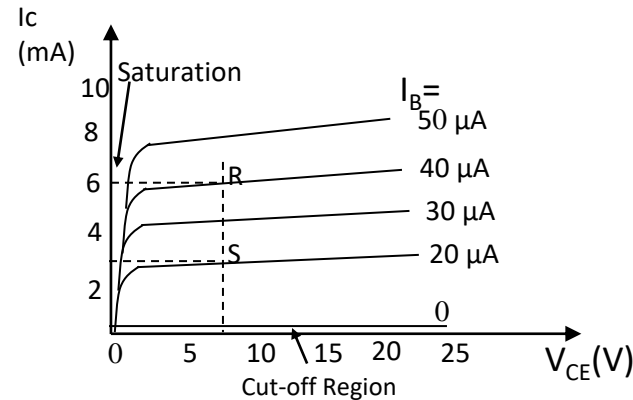


- Note:  $I_B$  in  $\mu A$  and  $I_C$  in mA
- (1) There is a threshold voltage (0.7 for Si, 0.3 for Ge) below which Base current is very small.
- (2) Can be used to find ac input resistance  $R_i = \Delta V_{BE} / \Delta I_B$ .  $R_i$  varies with location of operating point. Ranges from  $600\Omega$ - $4k\Omega$

- (1) Can be divided into 3 parts: saturation, active and cut-off regions.
- (2) Can be used to find ac output resistance  $R_o = \Delta V_{CE} / \Delta I_B$ . From  $10k\Omega$ - $50k\Omega$
- (3) Can find  $\beta$ . Ex: from points R and S  


$$\beta = (6-3)mA / (40-20)\mu A = 150$$

# Common-Collector Characteristics: NPN

  


- From before  $I_c = \beta I_B$
- but  $I_E = I_c + I_B = \beta I_B + I_B$
- $I_E = (\beta + 1) I_B$

## Input Characteristics

 

## Output Characteristics

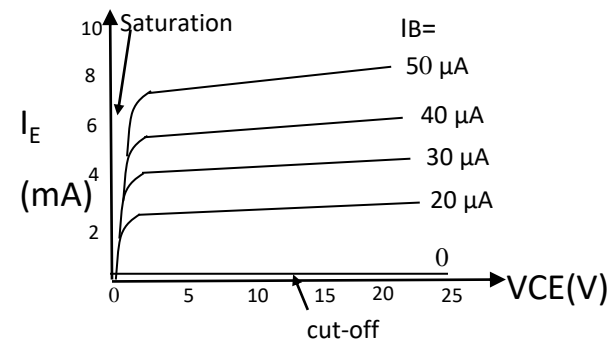

## Example 1

A transistor has  $I_{CBO} = 48 \text{ nA}$  and  $\alpha = 0.992$

1. Find  $\beta$  and  $I_{CEO}$
2. Find its exact collector current when  $I_B = 30 \text{ }\mu\text{A}$
3. Find the approximate collector current, neglecting leakage current


Required equations  $I_C = \alpha I_B / (1 - \alpha) + I_{CBO} / (1 - \alpha)$

$$\beta = \alpha / (1 - \alpha)$$


# Bias Circuits

- So far we considered bias in terms of adjusting the DC supply voltages.
- In practice we do this by having resistors in series with the DC supplies.
- We consider adjusting the value of bias
  - (a) to obtain specific values of input and output current and voltages,
  - (b) when we have achieved this we have set the **bias point**.

# Common-Base Bias Circuit:


 


- Input voltage no longer  $V_{EE}$  because there is a voltage drop across  $R_E$ .
- Similarly for output.
- But characteristics are still valid
- Kirchoff's Law for the output loop  $V_{cc} = I_c R_c + V_{CB}$
- Rearrange as:  $I_c = -(1/R_c)V_{CB} + V_{cc}/R_c$
- Consider  $I_c$  and  $V_{CB}$  as variables and  $V_{cc}$  and  $R_c$  as constants.
- This is an equation of a straight line with slope  $-1/R_c$  and intercepts  $V_{CB}=V_{cc}$  and  $I_c=V_{cc}/R_c$
- This is the load line for the transistor and can be plotted in the Common-Base output characteristics to find the point of intersection Q or Bias point.

 



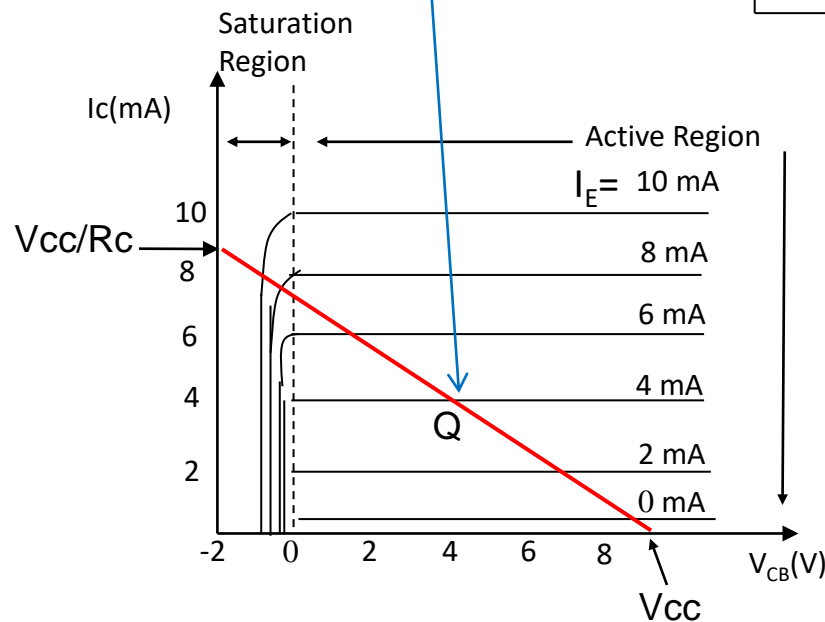 - To determine the point of intersection we need to know the current  $I_E$ .
- Most practical way is to regard the B-E junction as a FB diode having a voltage drop of 0.7V (for Si) and solve for diode current.
- This gives  $I_E = (V_{EE} - 0.7)/R_E$



- But transistor output characteristics are seldom used to design or analyze transistor circuits because transistors of the same type have a wide variation in their characteristics.
- The entire bias circuit is analyzed by a set of equations, which can solve for all the input and output current and voltages.


- **NPN C-B Circuit Equations:**

$$V_{BE} = 0.7 \text{ (Si), } 0.3 \text{ (Ge)}$$

$$I_E = (V_{EE} - V_{BE})/R_E$$

$$I_C = I_E - I_B \approx I_E$$

$$V_{CB} = V_{CC} - I_C R_C$$

 


- We can also get expressions for  $R_E$  and  $R_C$  from these equations to choose  $R_E$  and  $R_C$  values for desired input and output current and voltages.

$$R_E = (V_{EE} - V_{BE})/ I_E$$

$$R_C = (V_{CC} - V_{CB})/ I_C$$

## Example 2

 

Determine the

- 1) equation of the load line for the circuit for the Si transistor
- 2) Operating point



# Common-Emitter Bias Circuit

- It has only a single supply of voltage  $V_{CC}$ .
- \*  $R_B$  and  $R_C$  must be chosen so that, voltage drop across  $R_B >$  voltage drop across  $R_C$  to keep C-B junction RB.

$$V_{CC} = I_C R_C + V_{CE} \text{ or } I_C = (-1/R_C)V_{CE} + V_{CC}/R_C$$

We can again draw the load line on the output characteristics to find  $Q$  the bias point.

  - Need to know  $I_B$  to determine  $Q$
- $I_B$  is given by (diode circuit)  $I_B = (V_{CC} - V_{BE})/R_B$



- The set of equations are

### NPN C-E Circuit:

$$V_{BE} = 0.7 \text{ (Si)}, 0.3 \text{ (Ge)}$$



$$I_B = (V_{CC} - V_{BE}) / R_B$$

$$I_C = \beta I_B$$


$$V_{CE} = V_{CC} - I_C R_C$$

$$R_B = (V_{CC} - V_{BE}) / (I_C / \beta)$$

$$R_C = (V_{CC} - V_{CE}) / I_C$$

  


### Example 3

 

The Si transistor in the CE bias circuit has  $\beta=100$ .

Find the bias point

# Common-Collector Bias Circuit

 


- $V_{CC} = I_E R_E + V_{CE}$  or  $I_E = -(1/R_E)V_{CE} + V_{CC}/R_E$
- To find  $I_B$  to determine bias point (diode circuit)

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$\text{But } I_E = (\beta + 1)I_B$$

- Substitute and rearrange to get
 
$$I_B = (V_{CC} - V_{BE}) / [R_B + (\beta + 1)R_E]$$





- **NPN C-C Circuit**

$$V_{BE} = 0.7 \text{ (Si), } 0.3 \text{ (Ge)}$$

$$I_B = (V_{CC} - V_{BE}) / [R_B + (\beta + 1)R_E]$$


$$I_E = (\beta + 1) I_B$$

$$V_{CE} = V_{CC} - I_E R_E$$

$$R_E = (V_{CC} - V_{CE}) / I_E$$



$$R_B = (\beta + 1)(V_{CC} - V_{BE} - I_E R_E) / I_E$$
 
# BJT Transistor as a switch (BJT Inverter)





- Widely used in digital circuits and switching applications.
- We will consider the NPN inverter.
- Transistor is in C-E configuration.
- No bias voltage is connected to the base.
- $R_B$  is connected in series to base and then directly to a square or pulse type waveform that serve as inverter input.
- We make  $V_{cc} = V_{in}$
  
# BJT Transistor as a switch (BJT Inverter)





- When input to the inverter is High the B-E junction is FB and current flows through  $R_B$  to base.
- \*We choose  $R_B$  and  $R_C$  so that amount of base current flowing is enough to **saturate** the transistor ie: drive the transistor to the saturation region.
- The value of  $V_{CE}$  corresponding to this point called  $V_{CE(sat)}$  is very nearly zero (very small typically 0.1V). (see C-E charac. curve).
- Current at saturation point is called  $I_{C(sat)} \approx V_{CC}/R_C$ .
- When transistor is saturated it is said to be ON.
- Therefore High input to transistor results in Low output (0V).

  
# BJT Transistor as a switch (BJT Inverter)



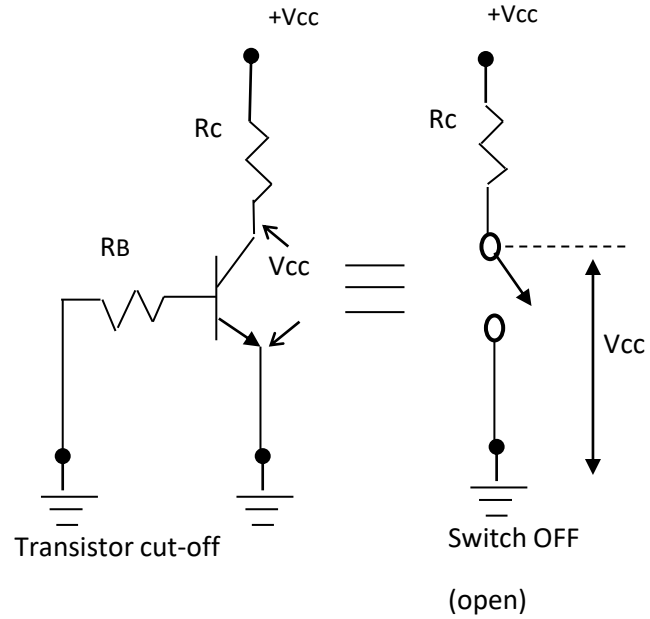 - When input to transistor is Low ie: 0V, B-E junction has no FB applied to it and hence no collector current flows.
- No voltage drop across  $R_c$ , and so  $V_{CE} = V_{CC}$ .
- In this situation transistor is in the cut-off region and is said to be OFF.
- A low input to the transistor results in a high output.






## AND Gate

 

Truth Table	A	B	Q
	0	0	0
	0	1	0
	1	0	0
	1	1	1

## OR Gate

   


Truth Table	A	B	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	1

# BJT Transistor as Amplifier

- Consider small signal operation which means that the output variations are small and that there is no change in the value of device parameters ( $\alpha$ ,  $\beta$  etc.).
- The transistor amplifier is studied from the standpoint of transistor behaviour as an AC amplifier.
- **Amplifier Gain:** AC voltage gain

- $$A_v = \Delta V_o / \Delta V_{in}$$

 


- For voltage amplifier  $A_v > 1$ .




- Only the AC components of the input and output are used to compute voltage gain.
- DC values have no bearing on the value of gain.
- AC current gain  $A_i = \Delta I_o / \Delta I_{in}$
- Device with  $A_i > 1$  is a current amplifier.
- It is possible to have  $A_v > 1$  and  $A_i < 1$ .
- Power Gain  $A_p = P_o / P_{in} = A_v A_i$

# Source Resistance:

 

- Every signal source has internal resistance called source resistance.
- If  $r_{in}$  is the amplifier input resistance,  $r_s$  and  $r_{in}$  are in series and form a voltage divider across the input of the amp.
- Input voltage  $v_{in} = [r_{in} / (r_s + r_{in})] v_s$
- Output voltage  $v_o = A_v v_{in}$
- Therefore  $v_o / v_s = A_v [r_{in} / (r_s + r_{in})]$  **\*\* (Edit in handout)**
- Thus the overall amp gain is reduced by a factor  $[r_{in} / (r_s + r_{in})] < 1$
- If  $r_{in} \gg r_s$  then  $[r_{in} / (r_s + r_{in})] \approx 1$  and there is little reduction in amp gain.
- Therefore **for a voltage amplifier it is desirable to have a large input resistance.**
- If current amplification is desired,  $i_o / i_s = A_i [r_s / (r_s + r_{in})]$ .
- Therefore the **current amplifier should have a small input resistance.**

## Load Resistance:

 

- If  $r_o$  is output resistance of amp

$$v_L = [R_L / (r_o + R_L)] v_o$$

- Therefore for a voltage amp  $r_o \ll R_L$  so that  $v_L = v_o$
- For current amp

$$i_L = [r_o / (r_o + R_L)] i_o$$

- Therefore for current amp  $r_o \gg R_L$

- When both source  $r_s$  and load  $R_L$  are taken into account
- Overall voltage gain

$$v_L / v_s = A_v [r_{in} / (r_s + r_{in})] [R_L / (r_o + R_L)]$$


- Overall current gain


$$i_L / i_s = A_i [r_s / (r_s + r_{in})] [r_o / (r_o + R_L)]$$

- If  $r_s$  is fixed, maximum power transferred from source to amp when  $r_{in} = r_s$
- Amp is matched to the source.
- If  $r_o$  is fixed, maximum power transferred to load when  $R_L = r_o$
- Amp matched to load.
 
## Purpose of Bias:


- In most single transistor amplifiers, the output voltage must always be +ve for NPN (or –ve for PNP).
- When this is the case, it is not possible for the output to be a pure AC waveform.
- The purpose of bias in a transistor amplifier is to set a DC **output level** somewhere in the middle of the total range of possible output voltages so that an AC waveform can be superimposed on it.
- The AC input causes the output voltage to vary above and below the bias voltage, but the instantaneous values of the output are always positive, in this example.



 


- Output voltage  $v_o = V_B + A \sin(\omega t)$  where  $V_B$  is bias voltage or DC component of the output.
- $A$  is the peak value of the sinusoidal AC output
- Values of  $V_B$  and  $A$  must be such that:  
 $V_B + A$  is not greater than maximum o/p voltage and  
 $V_B - A$  is not less than minimum o/p voltage.
- If this condition is not satisfied output voltage will reach its minimum or maximum extremes before the total AC variation take place.

 - Result is a flattening of the output signal which is called ‘clipping’.
- Purpose of AC amp is to have as output an amplified version of the input.
- Clipping distorts the output signal and is an example of amplitude distortion.



# Amplifier analysis:

 

- Small signal parameters are parameters whose values are determined under small signal (ac) operating conditions (we will use simple letters to signify ac).
- Ex:  $\beta = i_c/i_b \mid V_{CE}=\text{constant}$ ;  $\alpha = i_c/i_e \mid V_{CB}=\text{const.}$
- An important physical parameter is the small signal resistance from Emitter to Base called the emitter resistance  $r_e$

$$r_e = v_{be} / i_e \mid V_{CB} = \text{const}$$

\*  $r_e$  is the same as the Common-Base input resistance



- Since E-B junction can be seen as a FB diode an approximate value of  $r_e$  can be found (same as dynamic resistance of a diode),  $r_e = 0.026/I_E \Omega$ , where  $I_E$  is the DC emitter current.
- Small signal collector resistance  $r_c$  is the ac resistance from collector to base (output resistance in Common-Base).
- Because it is across a reverse bias junction  $r_c = v_{cb}/i_c \mid I_E=\text{const}$  it is of the order of several  $M\Omega$ .


  
## Equivalent Circuits: small signal model of transistor.


(We will only consider the simplified model that does not take into account reverse currents. There is a more accurate model called the Hybrid model)

- **C-B Amplifier Model:** All voltages and currents are ac quantities, all polarities periodically alternate.
- **Equivalent Circuit:** Circuit model for C-B Transistor.
- Figure shows that an increase in current into E is accompanied by an increase of current out of Collector.


 
## C-B Amplifier Model:


**ac Equivalent:** of that is external to transistor.



All DC sources (and C) are treated as ac short circuits to ground.

Replace transistor with small signal equivalent circuit.

 **Practical C-B Equivalent circuit** (// means in parallel)



- $R_E \gg r_e: r_e // R_E \approx r_e$

- $r_c \gg R_C: R_C // r_c \approx R_C$

- $v_s = v_{in} = i_e r_e$

- $v_o = i_c R_C = \alpha i_e R_C$


- but  $\alpha \approx 1, v_o = i_e R_C$

**Voltage Gain**  $A_v = v_o / v_{in} = \alpha R_C / r_e \approx R_C / r_e$

**Current Gain:**  $A_i = i_o / i_{in} = i_c / i_e = \alpha$


**C-B Amplifier with source and load:**

**ac equivalent:**

 

- $A_v = v_L / v_s = (R_C / r_e)[r_e / (r_s + r_e)][R_L / (R_C + R_L)]$
- $A_i = i_L / i_s = \alpha [r_s / (r_s + r_e)][R_C / (R_C + R_L)]$   
where  $i_s = v_s / r_s$

 **Common-Emitter Amplifier model:** Input resistance  $r_e$  drawn inside the emitter terminal to emphasize that it is an internal transistor parameter.



ac input resistance  $r_{in} = v_{be} / i_b$

But  $i_e = (\beta + 1) i_b$  which can be derived from the DC relations.

Then  $r_{in} = (\beta + 1) v_{be} / i_e$

But  $v_{be} / i_e = r_e$


Therefore  $r_{in} = (\beta + 1) r_e \approx \beta r_e$  as  $\beta \gg 1$

Equation shows that for C-E configuration input resistance is  $\beta$  times greater than C-B configuration.


Similarly, output resistance is  $\beta$  times smaller than C-B configuration.

\*Hence, C-E amplifier is inherently better suited for voltage amplification than the C-B counterpart (see slides 40 and 41).


## C-E Transistor Equivalent Model:

 

## C-E Amplifier

 


## Equivalent Circuit

 

- $r_e/\beta$  is in parallel with  $R_c$ .
  - In most practical circuits  $r_e/\beta \gg R_c$  so that  $r_e/\beta // R_c \approx R_c$
  - Therefore output resistance  $r_o = R_c$
  - Output voltage  $v_o = i_c r_o = \beta i_b R_c$ .
  - From equivalent circuit  $v_{in} = \beta r_e i_b$ .
  - Therefore voltage gain  $A_v = v_o/v_{in} = -R_c/r_e$
  - Negative sign inserted to show ac output is  $180^\circ$  out of phase with ac input.
- Current gain  $A_i = i_c/i_b = \beta$

## C-E Amplifier with source and load


 


- $v_L/v_s = A_v [(R_B//\beta r_e)/(r_s+R_B//\beta r_e)] [R_L/(R_L+R_C)]$  where  $A_v = -R_C / r_e$
- $i_L/i_s = A_i [(r_s//R_B)/(r_s//R_B+\beta r_e)][R_C/(R_L+R_C)]$
- **Effect of ac load resistance:** using load resistance terms only
- $A_{v_o} = v_L/v_s = - (R_C/r_e)[R_L/(R_L+R_C)] = - (1/r_e)[(R_L R_C/(R_L+R_C))]$   
 $= - (1/r_e)(R_L//R_C) = - r_L/r_e$

where  $r_L$  is ac load resistance.

- Therefore  $A_{v_o}$  is proportional to  $r_L = R_L//R_C$ .
- Since  $R_L//R_C < R_C$ , the effect of connecting a load  $R_L$  to the amplifier is to reduce the voltage gain

## Common-Collector Amplifier model:

  

- Collector shown grounded in ac equivalent as DC sources are treated as ac short circuits. Resistance between Base and Emitter is shown as  $\beta r_e \approx (\beta+1)r_e$ .
- The input resistance at the Base of the transistor (between Base and Ground)

$$r_{in} = v_{in} / i_{in} = v_{in} / i_b$$

$$v_{in} = i_b(\beta+1)r_e + i_e R_E \text{ (we have replaced } \beta \text{ with } \beta+1\text{).}$$

$$= i_b(\beta+1)r_e + (\beta+1)i_b R_E = i_b(\beta+1)(r_e + R_E).$$

$$\text{Therefore } r_{in} = [i_b(\beta+1)(r_e + R_E)] / i_b = (\beta+1)(r_e + R_E).$$

$$\text{Let } (\beta+1) \approx \beta \text{ so } r_{in} \approx \beta(r_e + R_E).$$

- In many practical circuits  $R_E \gg r_e$ . So  $r_{in} \approx \beta R_E$


- Voltage Gain  $A_v = v_o / v_{in} = i_e R_E / v_{in}$
- Substituting for  $v_{in}$  and simplifying  $A_v = R_E / (r_e + R_E)$
- Since  $r_e + R_E > R_E$  equation shows that the Common-Collector Amplifier always has a voltage gain  $< 1$
- Also as  $R_E \gg r_e$  then  $A_v \approx 1$  or  $v_o = v_{in}$
- Therefore the ac output voltage  $\approx$  ac input voltage in Common-Collector configuration.
- There is no phase change between the input and output and are separated only by the small resistance of the Forward Biased B-E junction.
- Since output voltage is the same as the input voltage in amplitude and phase, the Emitter is said to follow the Base and is known as the **Emitter Follower** rather than the Common-Collector.
- Current Gain  $A_i = i_e / i_b = (\beta + 1) \approx \beta$ . Therefore Current Gain can be  $\gg 1$  and so is the Power Gain  $A_p = A_v A_i \approx A_i$




# Field Effect Transistors (FETs)

- Like the BJT, **FET is a 3 terminal s-c device.**
- The current through a FET is due to either electrons **or** holes and therefore it is called a **unipolar** device.
- The current flow is controlled by an electric field set up in the device by an externally applied voltage.
- There are 2 main type of FETs:
  - (a) the **Junction Field Effect Transistor (JFET)** and
  - (b) the **Metal-Oxide-Semiconductor FET (MOSFET).**

# JFET:

 


- Consists of a N- type s-c bar with two P- type heavily doped regions diffused on opposite sides of its middle part.
- The two P sides are joined electrically and the common connection between them is called the **Gate (G)**.
- Electrical connections (called ohmic contacts) are made to both ends of the N- type s-c and are taken out in the form of two terminals called **Drain (D)** and **Source (S)**.
- The region of N material between the two P regions is called the **channel**.

 

- For a N- channel JFET, D is the terminal through which electrons leave the s-c bar and S is the terminal through which electrons enter the s-c.
- Thus conventional current flow is from D to S.
- The voltage applied to G controls the flow of current between D and S (by changing the channel width).
- (For a P channel JFET where current flow is due to holes, N-type heavily doped regions are diffused into a P-type s-c bar).

 
## Circuit Symbols for JFET:


- The symbols showing the G terminal off-center are used as a means of identifying the S: the S is the terminal closest to the G arrow.
- Some JFET are manufactured with D and S interchangeable and the symbols for these devices will have the G arrow in the center.


 
## Formation of depletion regions:




- In the N-channel JFET, the P-type G and N-type channel constitute a PN junction.
- In normal operation an external voltage  $V_{GS}$  is applied across G & S and a voltage  $V_{DS}$  applied across D & S.
- We first consider the case for when  $V_{DS} = 0$ .
- $V_{GS}$  is applied so that the PN junctions on each side of the channel are reverse biased.
- Thus G is made –ve with respect to S.
- The reverse bias causes a pair of depletion regions to form in the channel.






 

- Since the channel is more lightly doped than G, the depletion regions penetrate more into the N-type channel than into the P-type G.
- The width of the depletion region depends on the magnitude of the reverse bias voltage  $V_{GS}$ .
- The figure is for the case when  $V_{GS}$  is only a few tenths of a volt, so the depletion regions are relatively narrow.
- As  $V_{GS}$  is made more negative, the depletion region expand and the width of the channel decreases.
- The reduction in channel width increases the resistance of the channel and decreases the flow of current denoted as  $I_D$ .




- **The reverse bias across the G-S junction can also be achieved by applying a voltage  $V_{DS}$  across the D and S terminals.**
- As  $V_{DS}$  is increased (for  $V_{GS}=0$ ), the current  $I_D$  increase in direct proportion to it.
- As  $V_{DS}$  is increased further, noticeable depletion regions begin to form in the channel.
- The depletion region is broader near the D end of the channel than they are near the S end.

   

   

- This is because the current flowing through the channel creates a voltage drop along the length of the channel.
- When  $V_{DS}$  is increased further, the depletion region expand and the channel becomes very narrow near D, causing the total resistance of the channel to increase.
- As a consequence the current is no longer directly proportional to  $V_{DS}$  and instead the current begins to level off as shown in the middle figure.
- The figure on right shows what happens when  $V_{DS}$  is increased to a value large enough to cause the depletion regions to meet at a point near the channel Drain end.
- This condition is called **pinch-off**.




   


- At the point where pinch-off occurs the value of  $V_{DS}$  (the -ve of) is called pinch-off voltage  $V_P$ .
- $V_P$  is an important JFET parameter, whose value depend on the doping and the geometry of the device.
- $V_P$  is always -ve for an N channel JFET ( and +ve for P channel JFET).
- The middle figure show the current reaches a maximum value at pinch-off and that it remains at that value as  $V_{DS}$  is increased beyond  $V_P$ .
- This current is called the saturation current and designated  $I_{DSS}$ , the drain to source current with the gate shorted.

- We can get other characteristics figures by setting different values for  $V_{GS}$  as shown in figure.
- The set of curves are known as the **drain characteristics**.
- The dashed line which is parabolic joins the points on each curve where pinch-off occurs.
- A value of  $V_{DS}$  on the parabola is called a saturation voltage  $V_{DS(sat)}$ .
- At any value of  $V_{GS}$ , the corresponding value  $V_{DS(sat)}$  is the difference between  $V_{GS}$  and  $V_p$ :


$$V_{DS(sat)} = V_{GS} - V_p$$

 

 

- The equation of the parabola is  $I_D = I_{DSS} [V_{DS(sat)}/V_p]^2$
- The region to the right of the parabola is the pinch-off region (also known as the active or saturation region).
- This is the region in which the JFET is normally operated when used for small-signal amplification.
- The region to the left of the parabola is called the voltage-controlled resistance region, the ohmic region or the triode region.
- In this region the resistance is controlled by  $V_{GS}$ .
- The device acts like a voltage-controlled resistor in this region, and there are some practical applications that exploit this.

# Transfer Characteristics:

 


- Of a device is a plot of **output current** versus **input voltage**, for a **fixed value of output voltage**.
- When the input to a JFET is the gate-to-source voltage and the output current is drain current, the transfer characteristic can be derived from the drain characteristics.
- It is only necessary to construct a vertical line on the drain characteristics (a line of constant  $V_{DS}$ ) and to note the value of  $I_D$  at each intersection of the line with a line of constant  $V_{GS}$ .
- The values of  $I_D$  can then be plotted against the values of  $V_{GS}$  to construct the transfer characteristic, as shown in the figure for  $V_{DS}=8V$ .
- The choice of this value of  $V_{DS}$  means that all points are in the pinch-off region.
- The equation for the transfer characteristic in the pinch-off region is, to a close approximation,  $I_D = I_{DSS} (1 - V_{GS}/V_p)^2$


# MOSFET: The Metal-Oxide-Semiconductor FET

- Similar to the JFET
- Both have drain, gate and source terminals
- Both are devices whose channel conductivity is controlled by a gate-to-source voltage.
- The main difference between a MOSFET and JFET is the Gate terminal in a MOSFET is insulated from its channel region.
- For this reason, a MOSFET is also called an insulated-gate FET or IGFET.
- **MOSFETs come in two types: the depletion type and the enhancement type.**
- These names are derived from the two different ways that the conductivity of the channel can be altered by variations in  $V_{GS}$ .


# Depletion-Type MOSFETs

 

- N-channel, depletion type MOSFET.
- A block of high resistance, P type silicon forms a substrate, in which are
- embedded two heavily doped N type wells labeled N+.
- A thin layer of Silicon Dioxide ( $\text{SiO}_2$ ), which is an insulating material, is deposited along the surface.
- Metal contacts penetrate the  $\text{SiO}_2$  layer at the two N+ wells and become the drain and source terminals.
- Between the two N+ wells is a more lightly doped region of N material that forms the channel.
- Metal (Al) is deposited on the  $\text{SiO}_2$  opposite the channel and becomes the gate terminal.
- Note that the gate is insulated from the channel and that there is no PN junction formed between gate and channel.

 



- In normal mode of operation of a depletion-type N-channel MOSFET a voltage  $V_{DS}$  is connected between drain and source to make the drain +ve with respect to the source.
- The substrate is usually connected to the source as shown in the figure.
- When the gate is made negative with respect to the source by  $V_{GS}$ , the electric field it produces in the channel drives electrons away from a portion of the channel near the SiO<sub>2</sub> layer.
- This portion is thus depleted of carriers and the channel width is narrowed.
- The narrower the channel the greater its resistance and the smaller the current flow from drain to source.

 

- The device behaves like a N-channel JFET, the main difference being that the **channel width is controlled by the action of the electric field** rather than by the size of the depletion region of a PN junction.
- Since there is no PN junction  $V_{GS}$  can be made +ve without any concern for the consequence of the forward biasing a junction.
- Making  $V_{GS}$  +ve attracts more electrons into the channel and increases or enhances its conductivity.
- Thus the gate voltage can be made both +ve and –ve and the device can operate both in a depletion and enhancement mode.
- There is a PN junction between the N material and the P substrate but this junction is always reverse biased and very little substrate current flows. Thus the substrate has little bearing on the operation of the device.
- The resistance looking into the gate is very large, and of the order of thousands of megaohms.





# Enhancement –Type MOSFETs

  


- In the enhancement MOSFET there is no N-type material between the drain and the source (as found in the depletion MOSFET).
- Instead the P-type substrate extends all the way to the SiO<sub>2</sub> layer.
- Figure shows the normal electrical connections between D, G and S.
- As in the depletion MOSFET the substrate is usually connected to the source.
- Note that  $V_{GS}$  is connected so that the gate is +ve with respect to the source.
- The +ve gate voltage attracts electrons from the substrate to the region along the insulating layer opposite the gate.
- If the gate is made sufficiently +ve enough electrons will be drawn into that region to convert it into N type material.

# Enhancement –Type MOSFETs

  


- Thus a N type channel will be formed between drain and source and the P material is said to have been inverted to form an N type channel.
- If the gate is made still more +ve, more electrons will be drawn into the region and the channel will widen making it more conductive.
- Thus making  $V_{GS}$  more +ve, enhances the conductivity of the channel and increase the flow of current from drain to source.
- Since electrons are induced into the channel to convert it into N type material the device is also known as an induced N-channel enhancement type MOSFET.

# Circuit Symbols:

 

Depletion-Type

 

Enhancement-Type

# Advantages of N-channel MOSFETs over P-channel

- N-channel MOSFETs have become much more popular than P-channel.
- The main advantage of N-channel MOSFET, over P-channel, is due to the charge carriers in N-channel devices being electrons which have a mobility of about  $1300 \text{ cm}^2/\text{V.S}$  compared to the charge carriers in P-channel devices being holes which have a mobility of about  $500 \text{ cm}^2/\text{V.S}$ .
- Since the current in a s-c is directly proportional to the mobility, the current in a N-channel MOSFET is more than twice that of a P-channel with the same dimensions.
- The ON resistance of the N-channel MOSFET is  $1/3$  of that for P-channel.
- This means that in order to achieve the same value of current and ON resistance, the P-channel MOSFET requires 3 times the area of an equivalent N-channel MOSFET.
- Thus electronic circuits using N-channel MOSFETs are much smaller than circuits containing P-channel MOSFETs.